

Button with 2 LEDs (Switch Mode)

EXERCISE Try to turn on and off two LEDs using the state of one button.

HARDWARE REQUIRED

Arduino Board
momentary button or switch
10K ohm resistor
2 LEDs
2 220Ω Resistors
breadboard
hook-up wire

SCHEMATIC