

## Servo Sketch

*EXERCISE* Develop a project using an analog sensor (a potentiometer or a photocell) and a servo motor. You can use optional LEDs.

### *HARDWARE REQUIRED*

Arduino Board  
10K Potentiometer  
Potentiometer or Photocell  
Servo Motor

### *SCHEMATIC*