

Theramin

EXERCISE Play melody using Capacitive Sensor features. Use a digital circuit as an analogue device to produce sound. Buttons are also desirable.

HARDWARE REQUIRED

Arduino Board
momentary buttons or switch (optional)
10K ohm resistors (optional)
LEDs (optional)
220 Ω Resistors (optional)
M Ω Resistors
Metal foils or metal objects
buzzers or 8 Ω Speakers
breadboard
hook-up wire

SCHEMATIC