

Change the Blink Pulse Using Pot

EXERCISE Use a potentiometer to control the blinking pulse of an LED

HARDWARE REQUIRED

- Arduino Board
- 10K Potentiometer
- One (1) LED
- One 220 Ω Resistor
- Breadboard

SCHEMATIC